

Digital Logic Basics

Simplify the following Boolean expressions to a minimum number of literals:

1. $xy + xy'$
2. $xyz + x'y + xyz'$
3. $(A + B)'(A' + B)'$

Draw a circuit diagram for each of your answer to 1 a-c (5 points each)